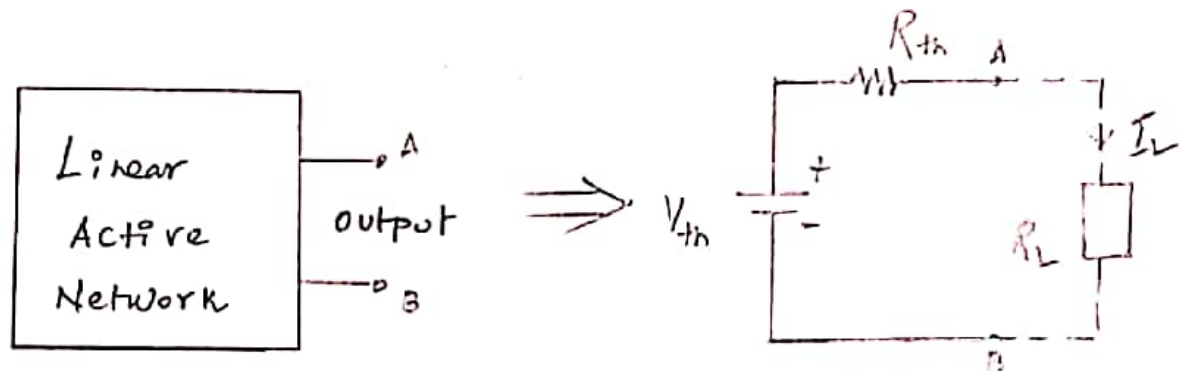


Thevenin's theorem

Statement: Any linear active network can be replaced by a single voltage source (V_{th}) in series with a single resistance (R_{th}).



Where,

V_{th} - Thevenin's Voltage

R_{th} - Thevenin's resistance

R_L - load resistance

I_L - load current

V_{oc} - open circuit voltage.

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$V_{th} = V_{oc}$$


Steps to find V_{th} & R_{th}

1. Remove R_L , mark the terminals A & B
2. Find V_{th}
3. Remove R_L , mark the terminal A & B

4. Kill the sources (oc the current source, open circuit the voltage source.)
short circuit the voltage source.)

5. Find R_{th} .

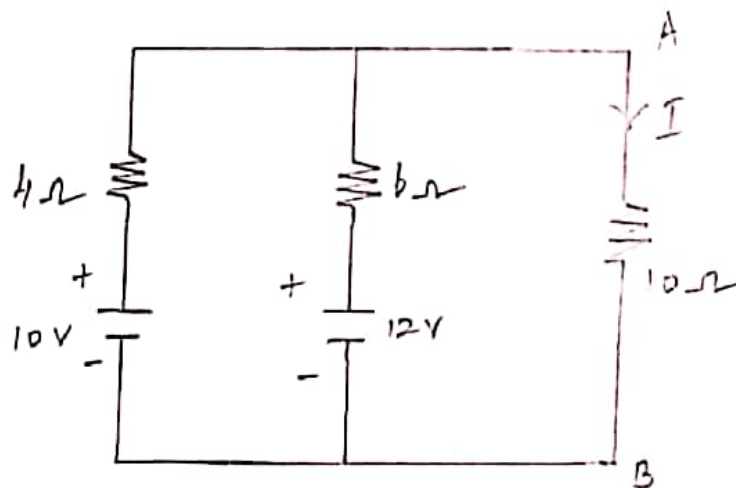1. Determine the current I in the network by using thevenin's theorem.




$$I = I_L$$

V_{th} :

1. Remove R_L , mark the terminals AB


2. Find V_{th}

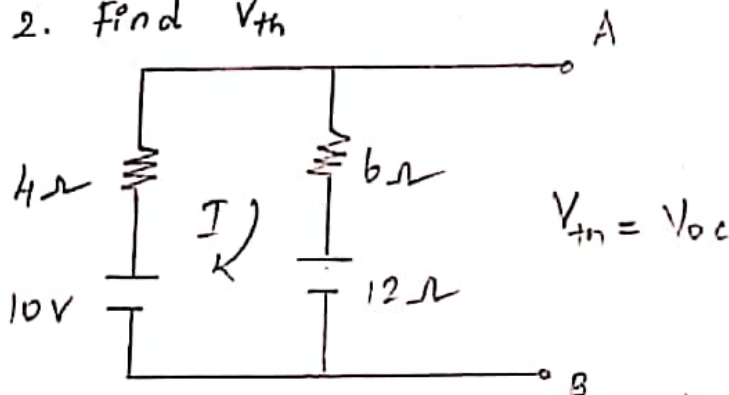

$$10 - 12 = 4I + 6I$$

$$-2 = 10I$$

$$\boxed{I = -0.2 \text{ A}}$$

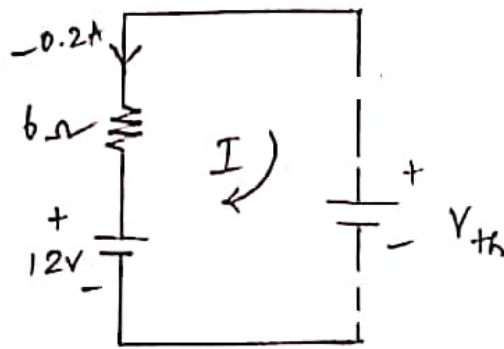

$$12 - V_{th} = 6I$$

$$12 - V_{th} = 6(-(-0.2))$$


$$-V_{th} = 1.2 - 12$$

$$-V_{th} = -10.8$$

$$V_{th} = 10.8 \text{ V}$$

R_{th} :

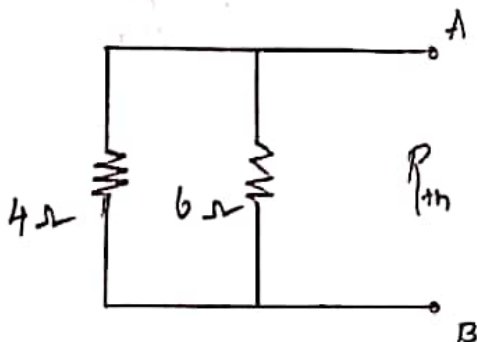1. Remove R_L mark terminals AB
2. Kill the sources (sc voltage source, oc current source)
3. Find R_{th}




$$R_{th} = \frac{4 \times 6}{4 + 6} = 2.4 \Omega$$

$$R_{th} = 2.4 \Omega$$


$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{10.8}{2.4 + 10} = 0.871 \text{ A}$$

$$I_L = 0.871 \text{ A}$$

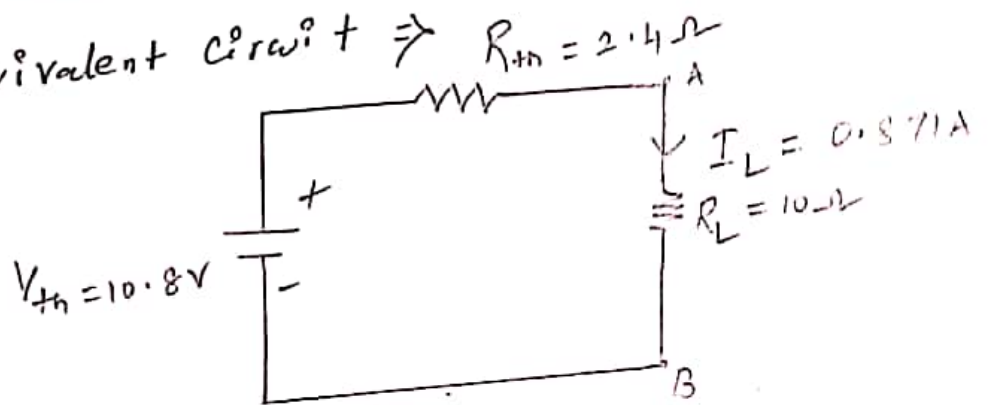Thevenin's equivalent circuit $\Rightarrow R_{th} = 2.4 \Omega$




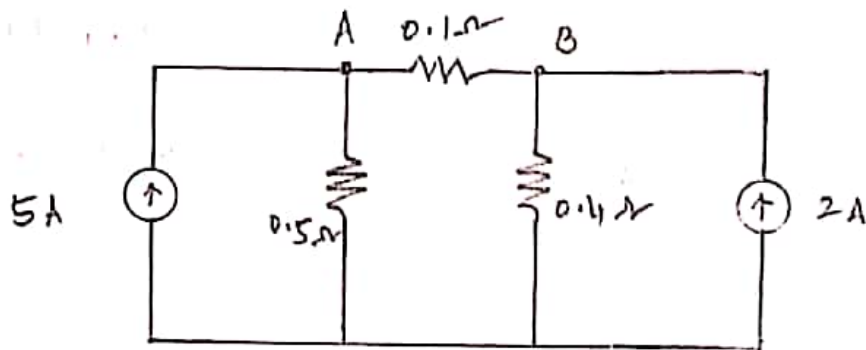
2. It's required to find current through the 0.1Ω resistor in the figure. Using thevenin's theorem.



V_{th} !

1. Remove R_L mark terminals A & B

2. Find V_{th}

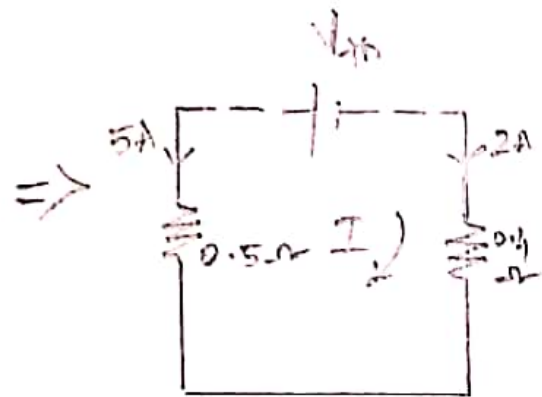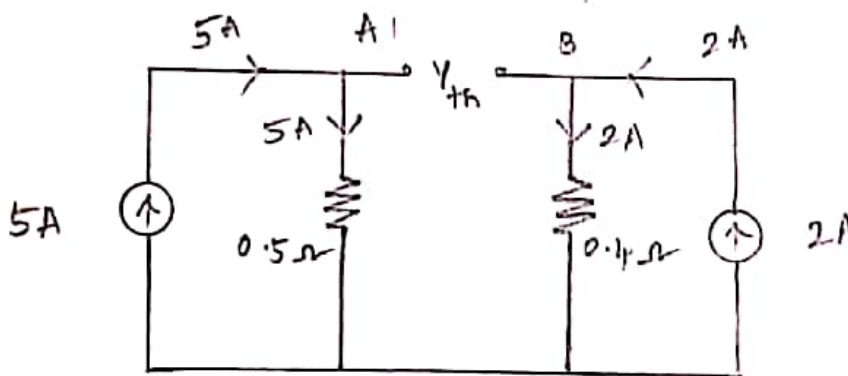

$$V_{th} = 0.5(-5) + 0.4(2) = -2.5 + 0.8 = -1.7$$


$$V_{th} = 1.7 \text{ V}$$

R_{th} !

Remove R_L , Mark terminals A & B


Kill sources (OC current source,
SC voltage source)

Find R_{th}

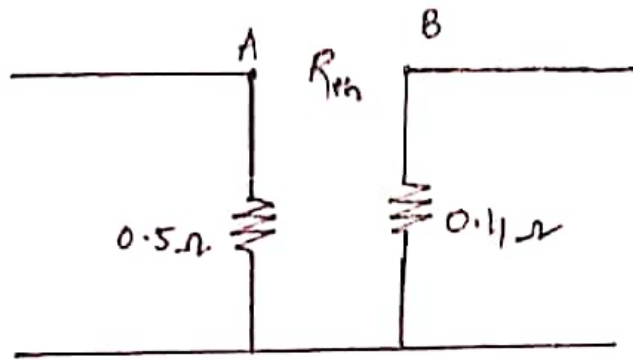

$$R_{th} = 0.5 + 0.4$$

$$R_{th} = 0.9 \Omega$$

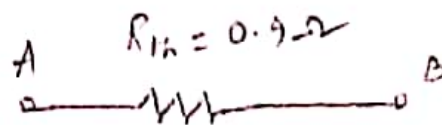

$$I_L = \frac{V_{th}}{R_L + R_{th}} = \frac{1.7}{0.1 + 0.9} = 1.7 \text{ A}$$

$$I_L = 1.7 \text{ A}$$

Thevenin's equivalent circuit

