


## Maximum power transfer theorem:

Statement: Maximum power will be delivered from source to load when ( $R_L$ ) load resistance is equal to thevenin's resistance ( $R_{th}$ ).


$$P_{max} = \frac{V_{th}^2}{4R_L}$$

when  $R_L = R_{th}$

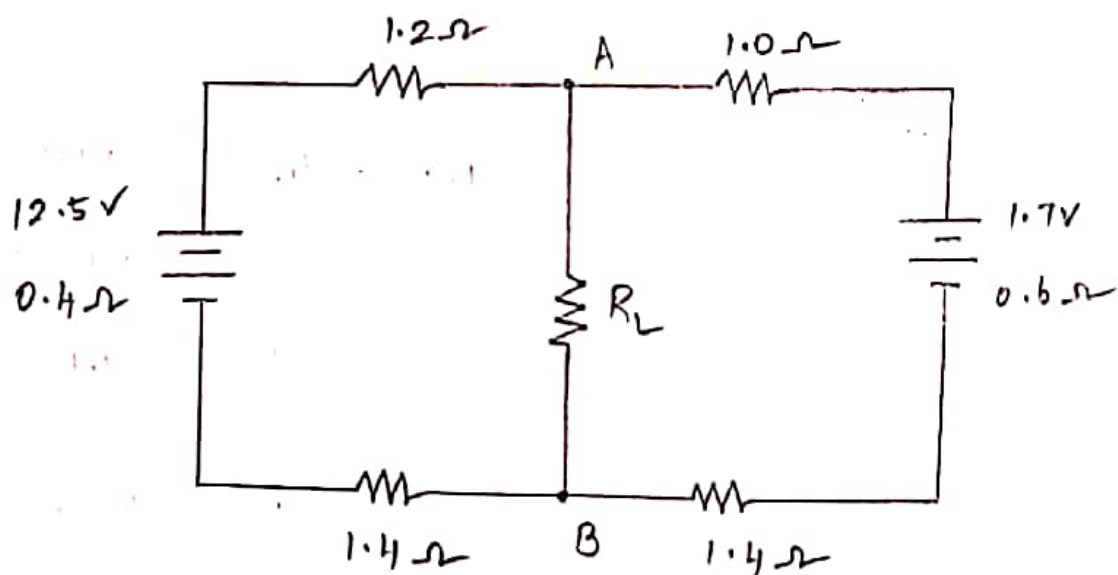1. For the circuit of the figure. Find the value of  $R_L$  for maximum power delivered to it. Calculate also the maximum load power.




$V_{th}$  !

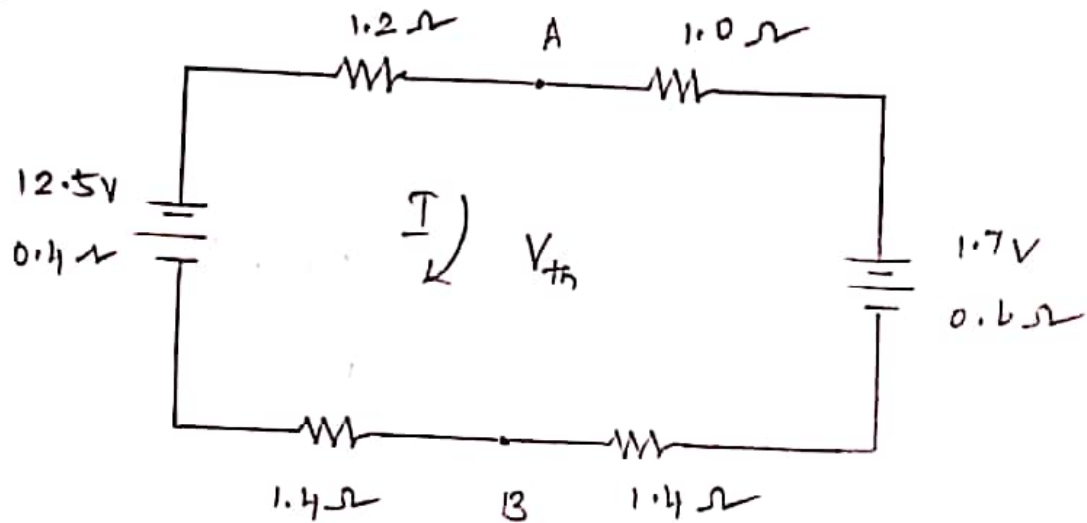

$$I = \frac{V}{R}$$

$$= \frac{12.5 - 1.7}{0.4 + 1.2 + 1.0 + 0.6 + 1.4 + 1.4}$$

$I = 1.8 \text{ A}$

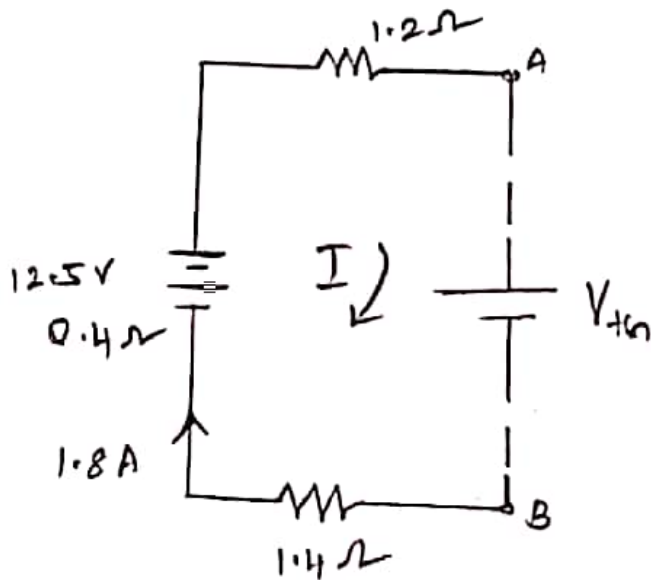


$$12.5 - V_{th} = 3 \times 1.8$$

$$= 5.4 - 12.5$$

$$-V_{th} = -7.1$$

$V_{th} = 7.1 \text{ V}$


$R_{th}$ :

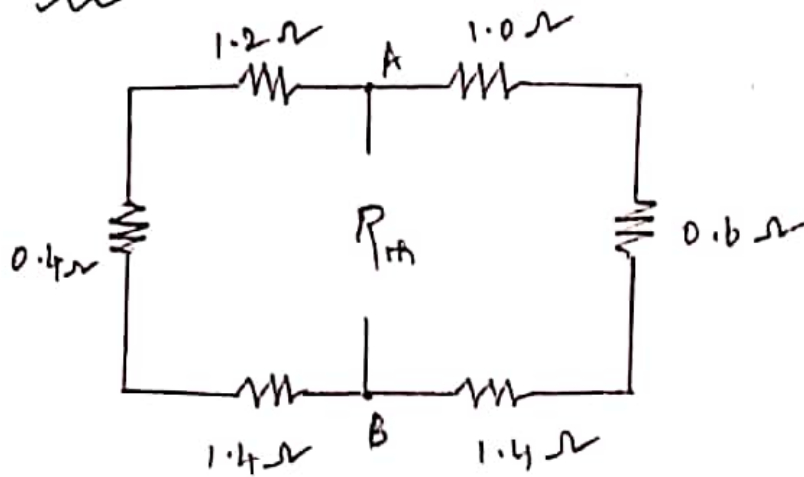

$$\Rightarrow 0.4 + 1.2 + 1.4 = 3$$


$$\Rightarrow 1.0 + 0.6 + 1.4 = 3$$

$\Rightarrow$

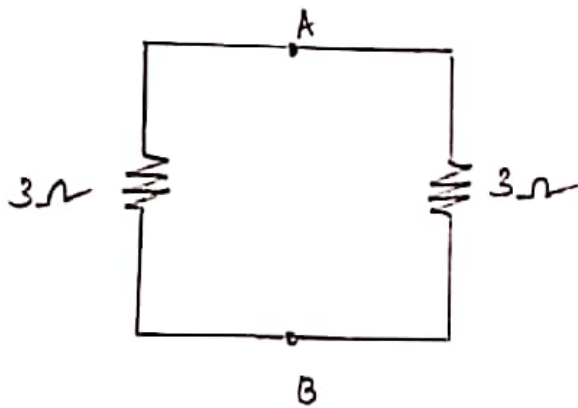

$$\frac{3 \times 3}{3 + 3} = \frac{9}{6} = 1.5\Omega$$

$\Rightarrow$

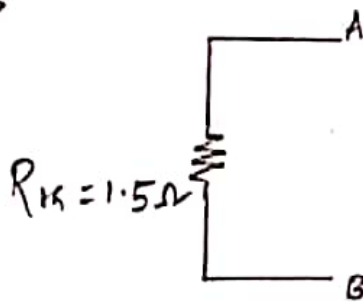


$$R_{th} = 1.5\Omega$$

$$R_L = R_{th}$$

$$P_{max} = \frac{V_{th}^2}{4R_L} = \frac{(7.1)^2}{4(1.5)} = \frac{50.41}{6} = 8.40 \text{ W}$$


$$P_{max} = 8.40 \text{ Watts}$$

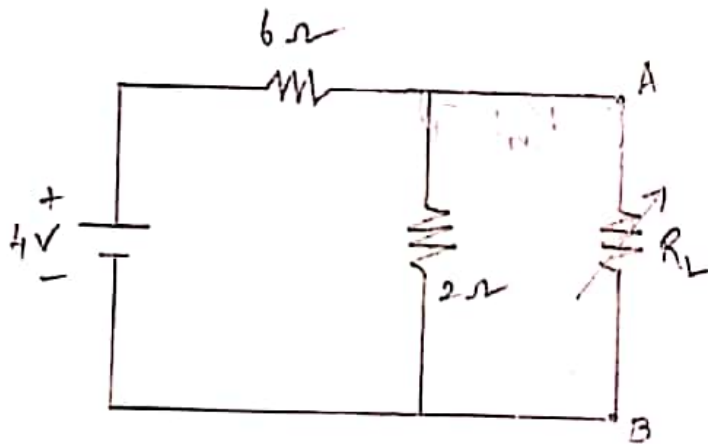2. Determine the value of load resistance  $R_L$  when it is dissipating maximum power. Also find the maximum power dissipated in the load resistance for the circuit given.



$V_{th}$  :

Remove  $R_L$  find  $V_{th}$

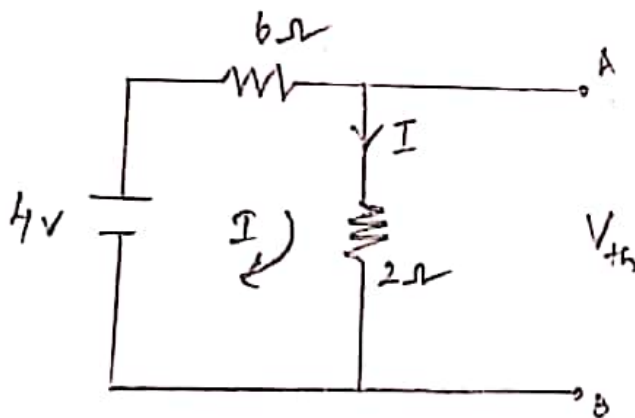


$$4 = 6I + 2I$$

$$4 = 8I$$

$$I = \frac{4}{8} = 0.5$$

$I = 0.5 \text{ A}$

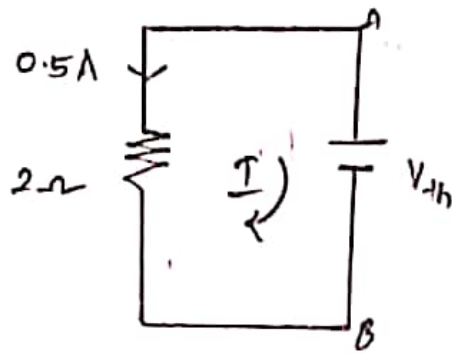


$$-V_{th} = 2(-0.5)$$

$$-V_{th} = -1$$


$$V_{th} = 1V$$

$R_{th}$ :

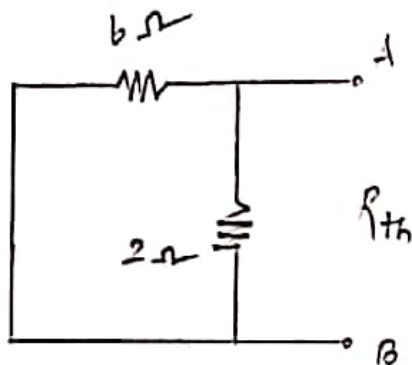

$$\frac{6 \times 2}{6 + 2} = \frac{12}{8} = 1.5\Omega$$

$$R_{th} = 1.5\Omega$$

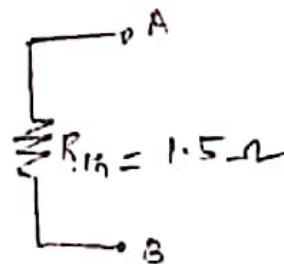

$$R_L = R_{th}$$

$$P_{max} = \frac{V_{th}^2}{4R_L} = \frac{1^2}{4(1.5)} = \frac{1}{6} = 0.1667 \text{ Watts}$$

$$P_{max} = 0.1667 \text{ Watts}$$