

18EES101J - Basic Electrical and Electronics Engineering

Unit - 1

Electric circuits (Dc circuits)

Current (I): Flow of electrons in a closed circuit.

Unit is ampere.

Voltage (V): The difference in potential between any two points is called voltage or potential difference.

Unit is Volt.

Power (P): It's the product of voltage and current.

Unit is Watts / kW

$$P = VI \text{ (Watt)}$$

Energy (E): It's the product of power and time

Unit is Watt Sec or (kWhr)

$$\text{Electrical Energy (E)} = P \times t \text{ (Wattsec)}$$

Resistance (R) :

It's the property of the conductor that opposes the flow of current through it.

Unit is ohm (Ω).

Ohm's Law:

At constant temperature the potential difference between two points is directly proportional to the current flowing through it.

$$V = IR$$

R & Temp (Constant)

R - Const

Where,

V - voltage

I - current

R - resistance

1. The current flowing through a resistor is 0.8 A when a potential difference of 20 V is applied.

What is the value of resistance

$$R = \frac{V}{I}$$

$$= \frac{20}{0.8}$$

$$R = 25\ \Omega$$

2. A source of emf of 15 V supplies a current of 2 A . How much energy is provided in this time ($t = 6\text{ mins}$).

$$P = VI$$

$$= 15 \times 2$$

$$P = 30\text{ Watts}$$

$$E = P \times t$$

$$= 30 \times (6 \times 60)$$

$$E = 10800\text{ Watt Sec}$$

3. Determine the power dissipated by an element of an electrical device of resistance 20Ω . when a current of $10A$ flows through it. If the device is on for 6 hrs, determine the energy used and the cost, if 1 unit of electricity costs 7 paise.

$$E = P \times t$$

$$P = V \times I$$

$$P = I^2 R$$

$$= 10^2 (20)$$

$$P = 2000 \text{ Watts or } 2 \text{ Kw}$$

$$E = 2 \text{ Kw} \times 6 \text{ hr}$$

$$E = 12 \text{ Kw hr}$$

$$1 \text{ unit of electricity} = 1 \text{ Kw hr}$$


$$\begin{array}{l} \text{Hence number of} \\ \text{units used} \end{array} = 12$$

$$\text{Cost of Energy} = 12 \times 7 = 84 \text{ Paise.}$$

Kirchhoff's Voltage Law (KVL)

In a closed loop the algebraic sum of potential differences is zero.

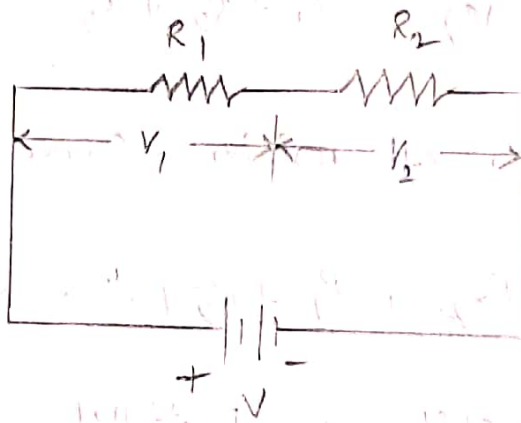In a closed loop the sum of potential rises is equal to sum of potential drops.




$$V = V_1 + V_2$$

Kirchhoff's Current Law (KCL)

The algebraic sum of currents meeting at a junction is zero.


The sum of incoming currents is equal to outgoing currents.

Currents.

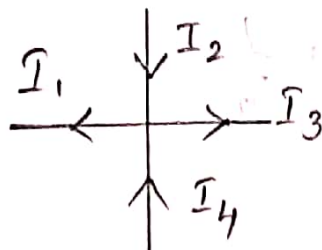

$$I_1 + I_3 = I_2 + I_4$$

Resistors Connected in Series

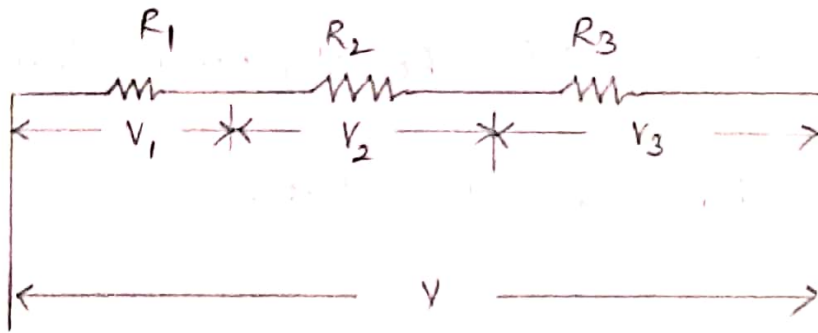

Equivalent Resistance


$$R_{eq} = R_1 + R_2 + R_3$$

$$V = V_1 + V_2 + V_3$$

For n -number of resistors connected in series, then

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Resistors Connected in parallel

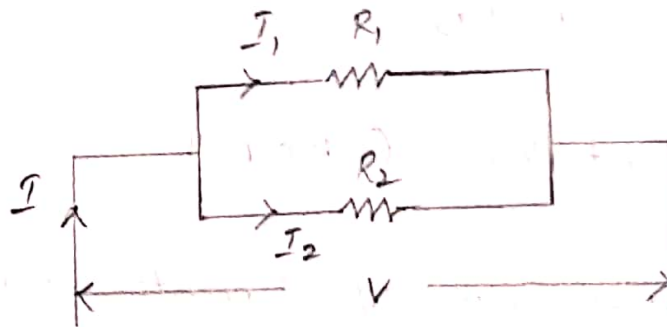


$$I = I_1 + I_2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Voltage division rule:

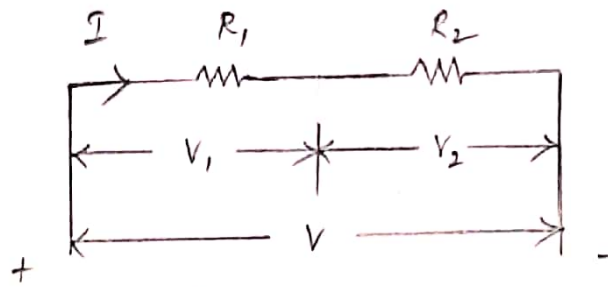Consider two resistors connected in series



$$V_1 = I R_1$$

$$V_2 = I R_2$$

Apply KVL

$$V = V_1 + V_2$$

$$= I R_1 + I R_2$$

$$V = I (R_1 + R_2)$$


$$I = \frac{V}{R_1 + R_2}$$

Total voltage V is dropped in two resistors

$$\text{Voltage across element} = \text{Total voltage} \times \frac{\text{Voltage across same resistance}}{\text{Total resistance}}$$

$$\therefore \begin{array}{l} V_1 = V \frac{R_1}{R_1 + R_2} \\ V_2 = V \frac{R_2}{R_1 + R_2} \end{array}$$

Current division rule :

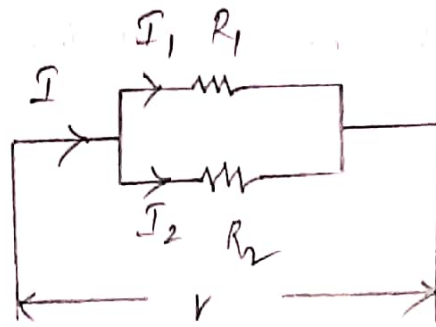


Consider two resistors are connected in parallel


Current through the element = Total current $\times \frac{\text{current through opposite resistance}}{\text{total resistance}}$

$I_1 = I \frac{R_2}{R_1 + R_2}$
$I_2 = I \frac{R_1}{R_1 + R_2}$

Star - Delta - Star Transformation

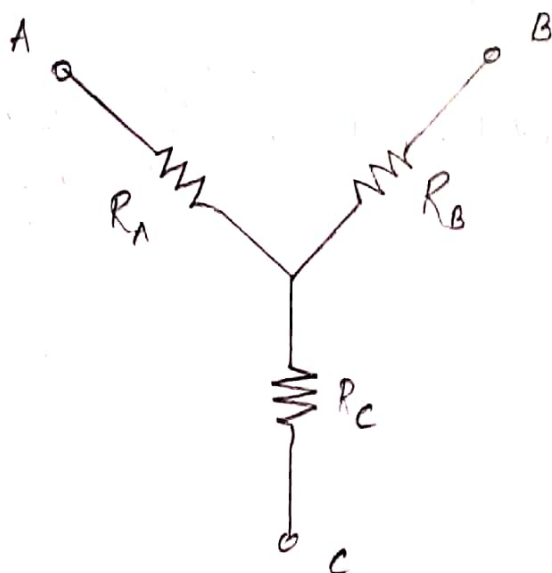

Star Connection

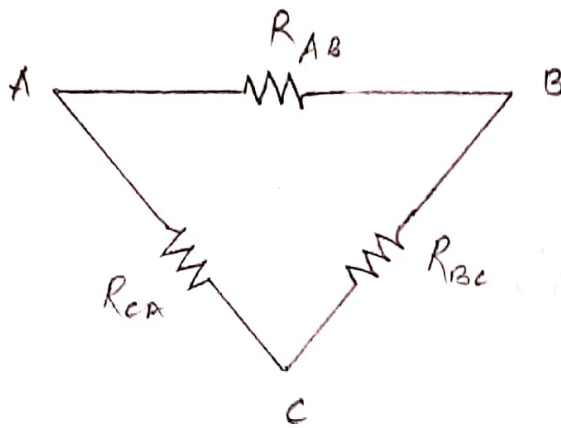

Delta Connection

Star (Y) to Delta (Δ)
 ~~~~~

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

If three resistance are equal  
 then,

$$R_A = R_B = R_C = R$$

$$R_{AB} = R_{BC} = R_{CA} = 3R$$

(Δ) (Y)  
Delta to Star :

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_C = \frac{R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$




If three resistances are equal

then,


$$R_{AB} = R_{BC} = R_{AC} = R$$

$$R_A = R_B = R_C = R/3$$

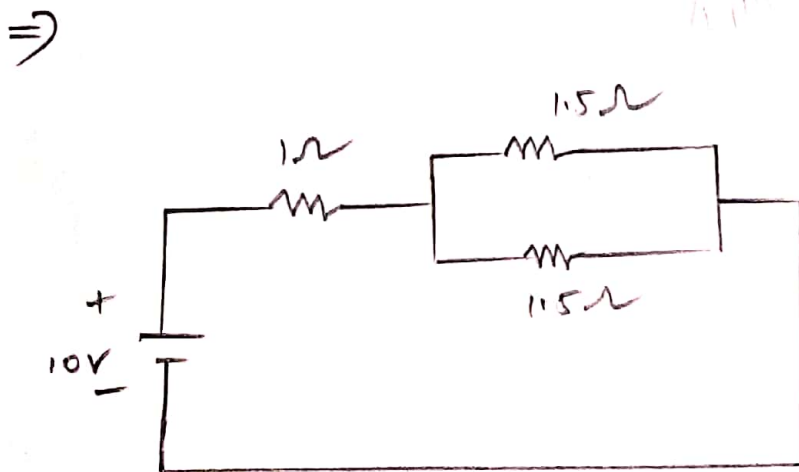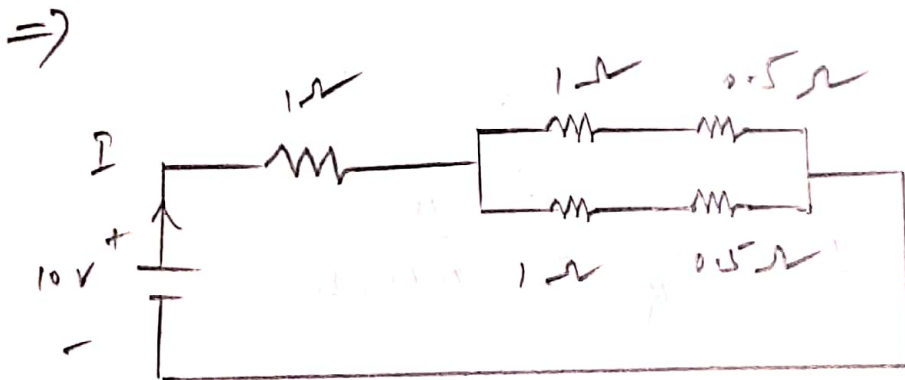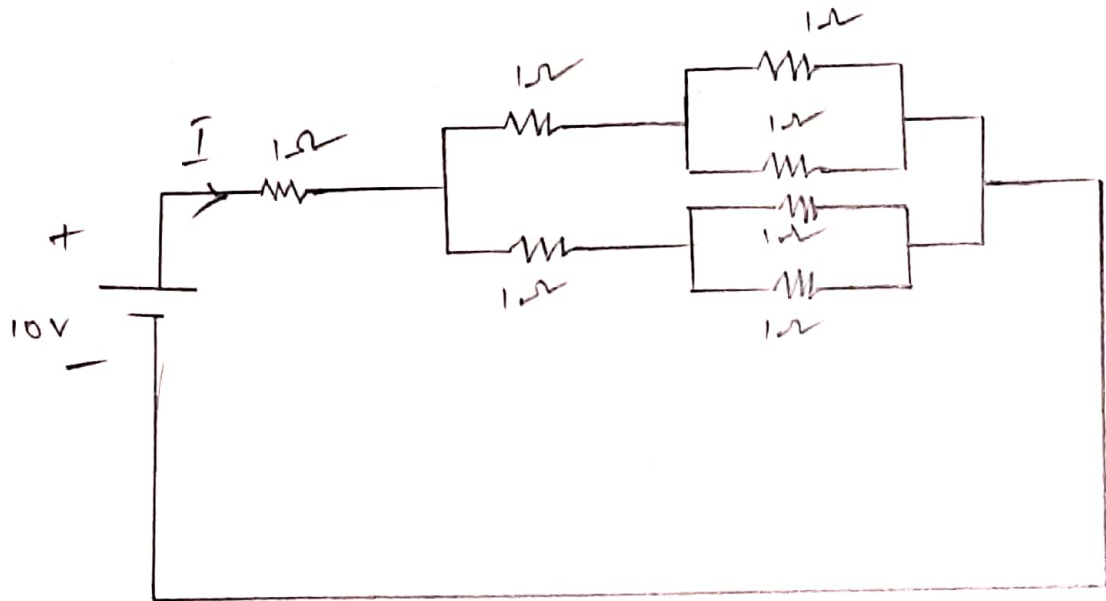
- ① All the resistances in Fig are  $1\Omega$  each. Find the value of current  $I$ .



$\Rightarrow$

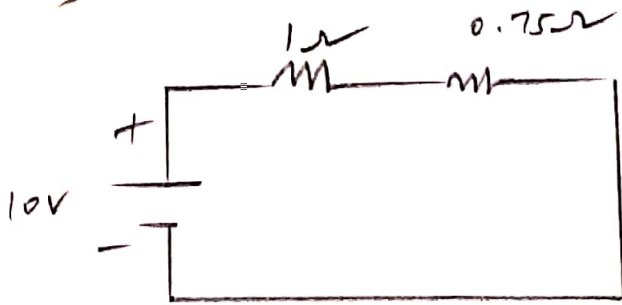


$\Rightarrow$

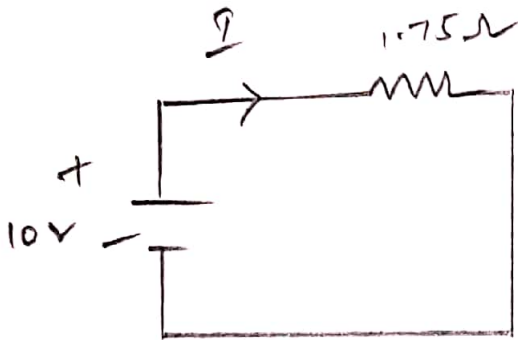

$$\text{Current } I = \frac{V}{R} = \frac{10}{1.75\Omega}$$

$$I = 5.714 \text{ A}$$

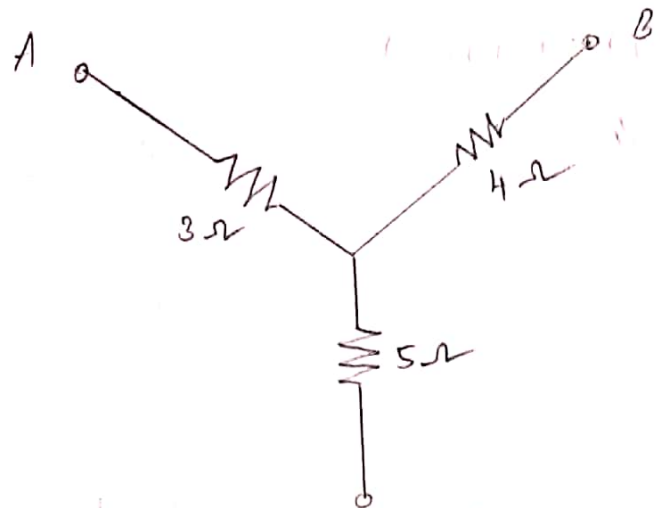1. Convert the star circuit into delta circuit.



$$\begin{aligned} R_{AB} &= \frac{R_A R_B + R_B R_C + R_C R_A}{R_C} \\ &= \frac{(3)(4) + (4)(5) + (5)(3)}{5} \\ &= \frac{12 + 20 + 15}{5} \\ &= \frac{47}{5} \end{aligned}$$

$$R_{AB} = 9.4 \Omega$$

$$\begin{aligned} R_{BC} &= \frac{R_A R_B + R_B R_C + R_C R_A}{R_A} \\ &= \frac{(3)(4) + (4)(5) + (5)(3)}{3} \\ &= \frac{47}{3} \end{aligned}$$


$$R_{BC} = 15.67 \Omega$$

$$R_{CA} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_B}$$


$$= \frac{(3)(4) + (4)(5) + (5)(3)}{4}$$

$$= \frac{47}{4}$$

$$R_{CA} = 11.75 \Omega$$

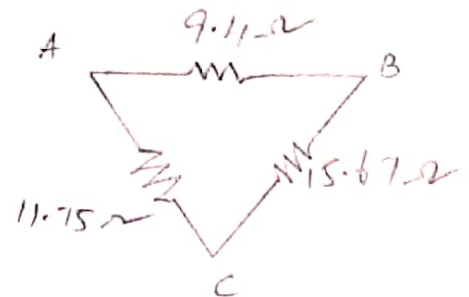

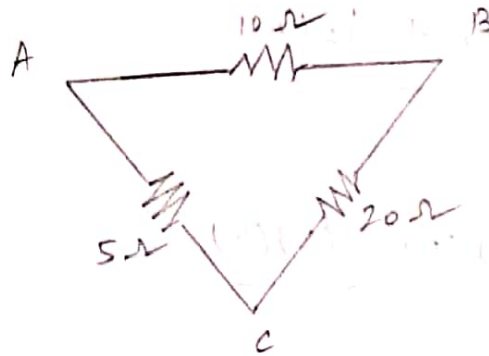2. Convert the delta circuit into star circuit.



$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$= \frac{10 \times 5}{5 + 10 + 20}$$

$$= \frac{50}{35}$$

$$R_A = 1.43 \Omega$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$= \frac{(10)(20)}{5 + 10 + 20}$$

$$= \frac{100}{35}$$


$$R_B = 5.714 \, \Omega$$

$$R_C = \frac{R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$


$$= \frac{(20)(5)}{5 + 10 + 20}$$

$$R_C = \frac{100}{35}$$


$$R_C = 2.86 \, \Omega$$

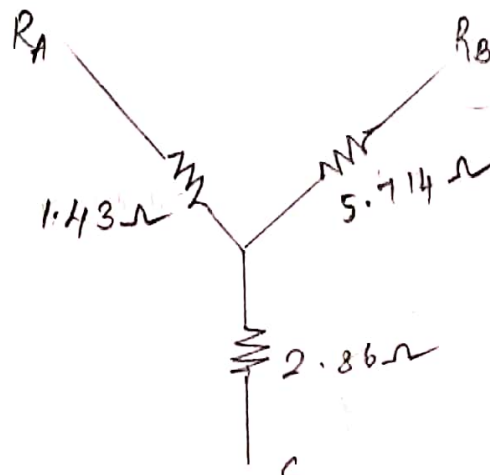

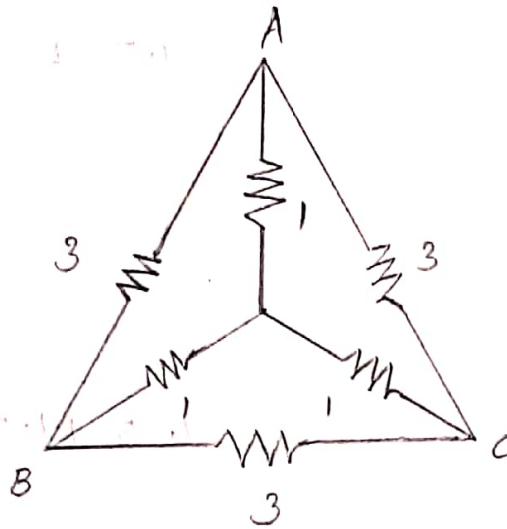3. For the network shown in figure, find the equivalent resistance b/w the terminals B & C. All resistance values are in ohm.



⇒

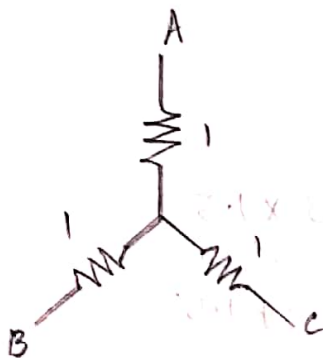

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$= \frac{1 + 1 + 1}{1}$$

$$R_{AB} = 3 \Omega$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A} = \frac{1 + 1 + 1}{1}$$


$$R_{BC} = 3 \Omega$$

$$R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B} = \frac{1 + 1 + 1}{1}$$

$$R_{CA} = 3 \Omega$$




⇒

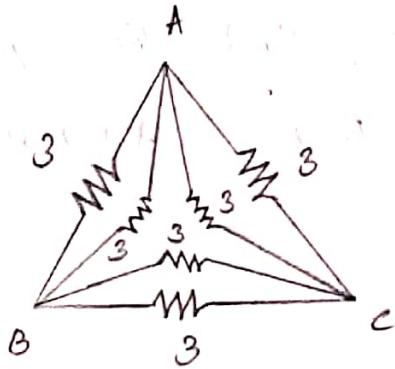

$$= \frac{3 \times 3}{3 + 3} = \frac{9}{6}$$

$$= 1.5 \Omega$$


⇒

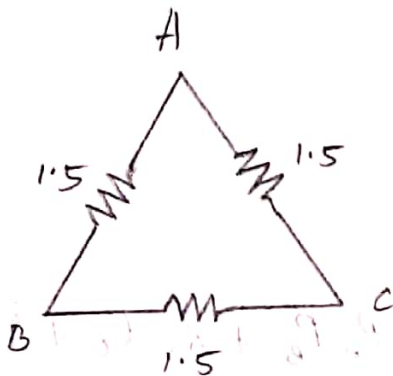

$$= 1.5 + 1.5$$

$$= 3 \Omega$$

⇒

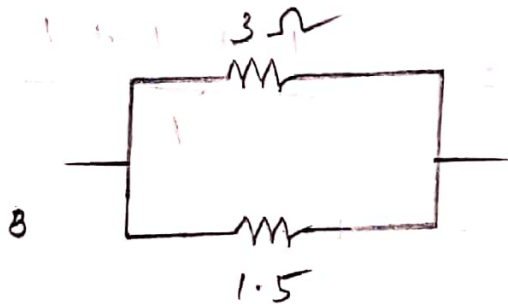


$$= \frac{3 \times 1.5}{3 + 1.5}$$

$$= \frac{4.5}{4.5}$$

$$= 1 \Omega$$



⇒

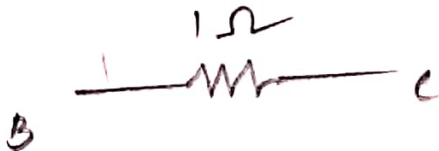


Equivalent resistance  
b/w B & C

$$R_{BC} = 1 \Omega$$

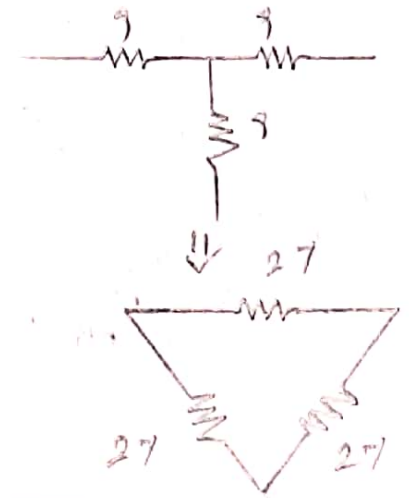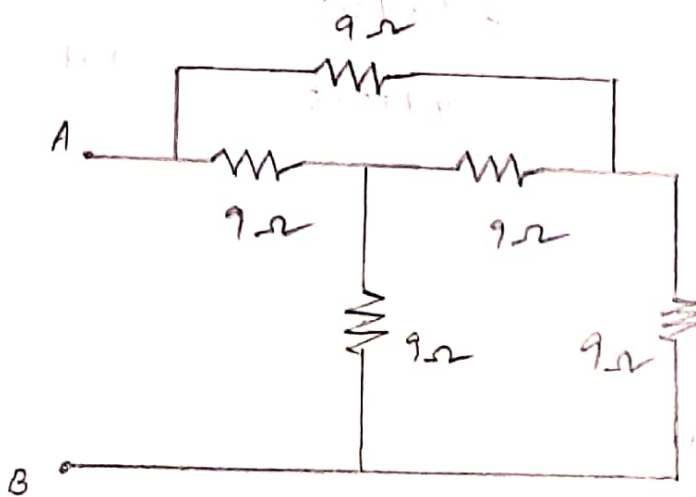4. Determine the equivalent resistance. All resistance values are in ohm.




$\Rightarrow$

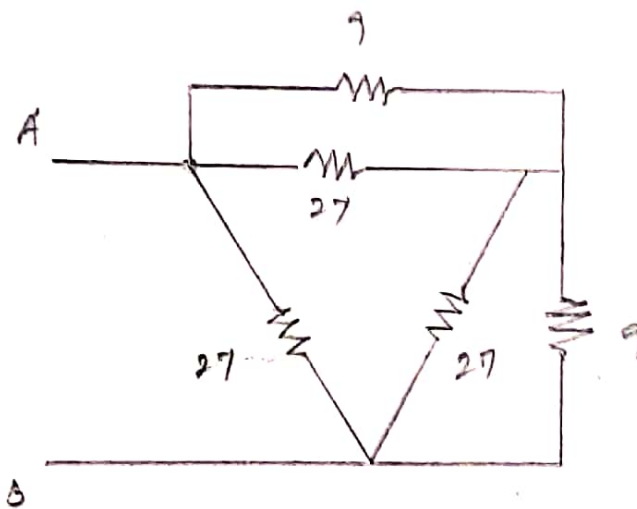


$$\frac{27 \times 9}{27 + 9} = 6.75\Omega$$


$$\frac{27 \times 9}{27 + 9} = 6.75\Omega$$

$\Rightarrow$

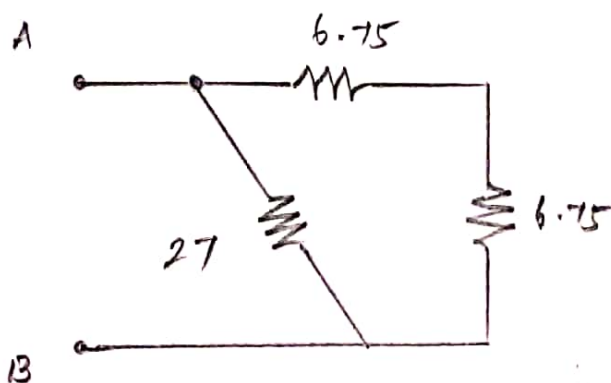

$\Rightarrow$

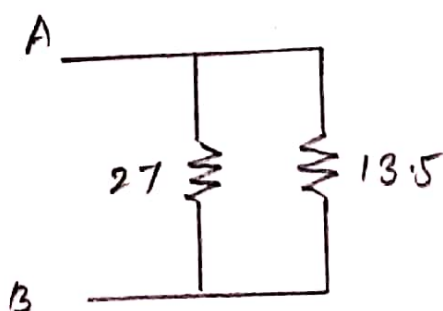

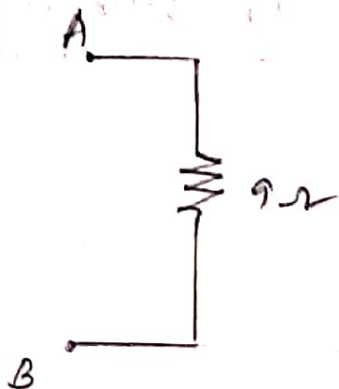

$$\frac{27 \times 13.5}{27 + 13.5} = 9\Omega$$


$$R_{AB} = 9\Omega$$

## V - I Relationship of circuit elements

| Circuit Elements | Voltage                     | Current                     | Power                  |
|------------------|-----------------------------|-----------------------------|------------------------|
| $R(\Omega)$      | $V = IR$                    | $I = \frac{V}{R}$           | $P = VI$               |
| $L(H)$           | $V = L \frac{di}{dt}$       | $i = \frac{1}{L} \int v dt$ | $P = Li \frac{di}{dt}$ |
| $C(F)$           | $V = \frac{1}{C} \int i dt$ | $i = C \frac{dv}{dt}$       | $P = Cv \frac{dv}{dt}$ |
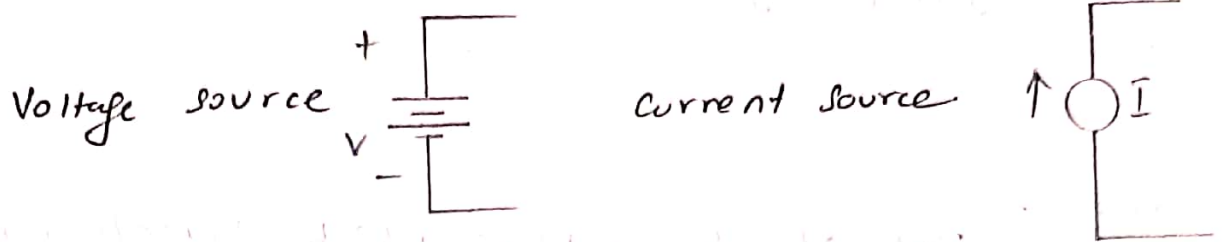
## Active elements:


The source of energy is called active element.




## Passive elements:

elements which dissipate energy

Resistance 

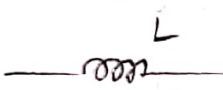Inductance 


Capacitance 

## Mesh:

A mesh is a loop that does not contain other loops.  $ABED$ ,  $BCFE$  are meshes.
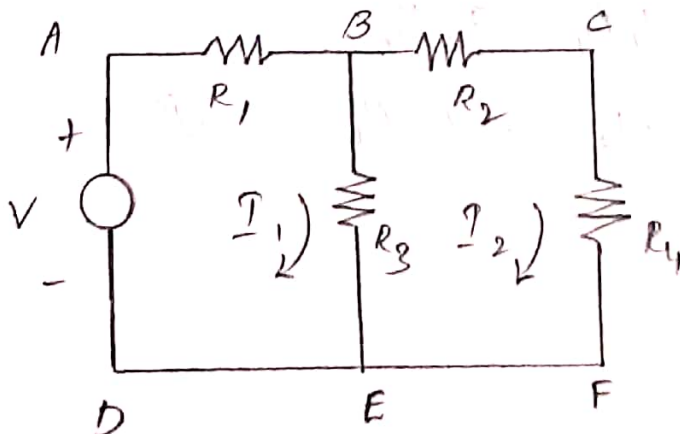
## Loop:


A loop is any closed path of branches.  
 $ABED$ ,  $BCFE$ ,  $ABCFED$ .



Node: The point at which two or more elements joined together is called node.

Branch: Part of the network which connects various points of the network.

Mesh analysis (loop current method)

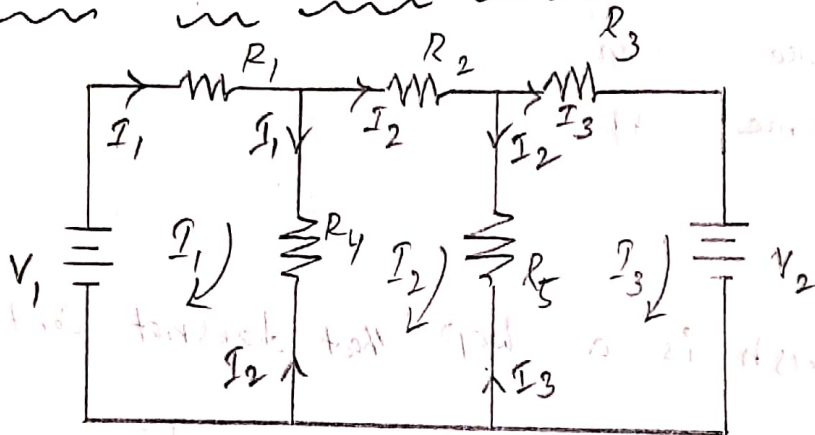

Loop : 1

Apply KVL

$$V_1 = I_1 R_1 + (I_1 - I_2) R_4$$

$$= I_1 R_1 + I_1 R_4 - I_2 R_4$$

$$V_1 = I_1 (R_1 + R_4) - I_2 R_4 \quad \text{--- (1)}$$

Loop: 2

~~~~

$$0 = (I_2 - I_1) R_4 + I_2 R_2 + (I_2 - I_3) R_5$$

$$0 = I_2 R_4 - I_1 R_4 + I_2 R_2 + I_2 R_5 - I_3 R_5$$

$$0 = -I_1 R_4 + I_2 (R_2 + R_4 + R_5) - I_3 R_5 \quad \text{--- (2)}$$

Loop: 3

~~~~


$$-V_2 = (I_3 - I_2) R_5 + R_3 I_3$$

$$-V_2 = -I_2 R_5 + I_3 (R_3 + R_5) \quad \text{--- (3)}$$

$$\begin{bmatrix} V_1 \\ 0 \\ -V_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_4 & -R_4 & 0 \\ -R_4 & R_2 + R_4 + R_5 & -R_5 \\ 0 & -R_5 & R_3 + R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{vmatrix} \quad \begin{aligned} I_1 &= \frac{\Delta_1}{\Delta} \\ I_2 &= \frac{\Delta_2}{\Delta} \\ I_3 &= \frac{\Delta_3}{\Delta} \end{aligned}$$

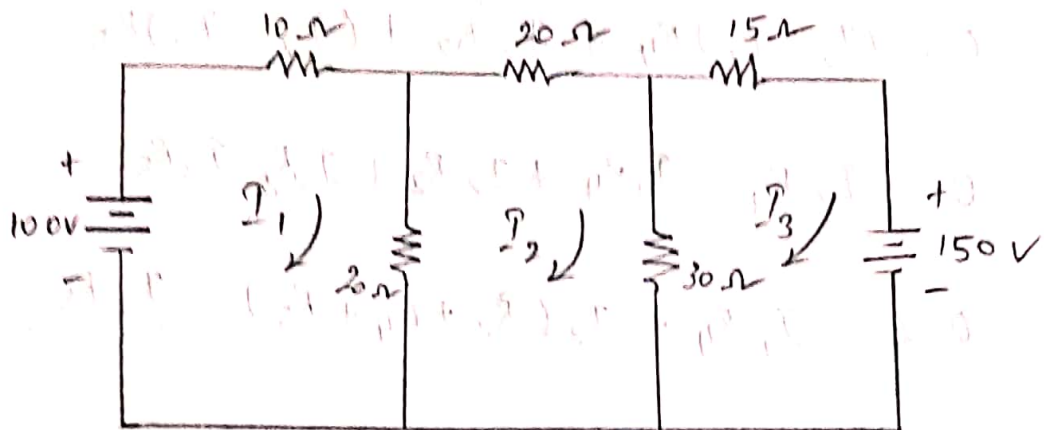1. Using mesh analysis, find mesh current in each loop for the given network.



loop: 1

Apply KVL

$$100 = 10I_1 + 20(I_1 - I_2)$$

$$100 = 10I_1 + 20I_1 - 20I_2$$

$$100 = 30I_1 - 20I_2 \quad - (1)$$

loop: 2

$$0 = 20(I_2 - I_1) + 20I_2 + 30(I_2 - I_3)$$

$$0 = 20I_2 - 20I_1 + 20I_2 + 30I_2 - 30I_3$$

$$0 = -20I_1 + 70I_2 - 30I_3 \quad - (2)$$

loop: 3

$$-150 = 30(I_3 - I_2) + 15I_3$$

$$-150 = 30I_3 - 30I_2 + 15I_3$$

$$-150 = -30I_2 + 45I_3 \quad - (3)$$



$$\begin{bmatrix} 100 \\ 0 \\ -150 \end{bmatrix} = \begin{bmatrix} 30 & -20 & 0 \\ -20 & 70 & -30 \\ 0 & -30 & 45 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 30 & -20 & 0 \\ -20 & 70 & -30 \\ 0 & -30 & 45 \end{vmatrix}$$

$$= 30((70 \times 45) - (-30 \times -30)) - (-20)((-20 \times 45) - (0 \times -30)) + 0$$

$$= (94500 - 27000) + 20(-900)$$

$$= 67500 - 18000$$

$$\boxed{\Delta = 49,500}$$

$$\Delta_1 = \begin{vmatrix} 100 & -20 & 0 \\ 0 & 70 & -30 \\ -150 & -30 & 45 \end{vmatrix} = 100((70 \times 45) - 900) + 20(0 - (-30 \times -150)) + 0$$

$$= 225000 - 20(4500)$$

$$= 225000 - 90000$$

$$\boxed{\Delta_1 = 135000}$$

$$\Delta_2 = \begin{vmatrix} 30 & 100 & 0 \\ -20 & 0 & -30 \\ 0 & -150 & 45 \end{vmatrix} = 30(0 - 4500) - 100(-20 \times 45 - 0) + 0$$

$$= 30(-4500) - 100(-900)$$

$$= -135000 + 90000$$

$$\Delta_2 = -45000$$

$$\Delta_3 = \begin{vmatrix} 30 & -20 & 100 \\ -20 & 70 & 0 \\ 0 & -30 & -150 \end{vmatrix} = 30(70 \times -150) + 20(-20 \times -150) - 0$$

$$+ 100(-20 \times -30) + 0$$

$$= 30(-10500) + 20(+3000) - 0 + 100(600)$$

$$= -315000 + 60000 + 60000$$

$$\Delta_3 = -195000$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{135000}{49500}$$

$$I_1 = 2.73 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-45000}{49500}$$


$$I_2 = -0.909 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-195000}{49500}$$

$$I_3 = -3.94 \text{ A}$$

In loop 2 & 3 the assumed current direction is opposite.  
(anti clock wise  $\rightarrow I_2$  &  $I_3$ )

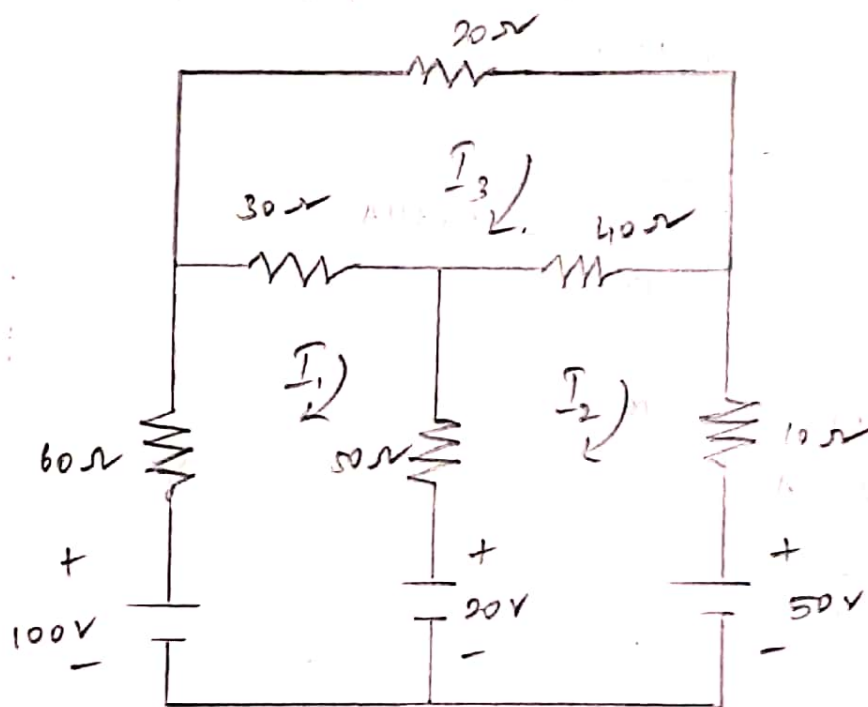2. Find the loop currents for the given network using mesh analysis.



$$\begin{bmatrix} 100 - 20 \\ 20 - 50 \\ 0 \end{bmatrix} \begin{bmatrix} 60 + 30 + 50 & -50 & -30 \\ -50 & 50 + 40 + 10 & -40 \\ -30 & -40 & 20 + 30 + 40 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} 80 \\ -30 \\ 0 \end{bmatrix} \begin{bmatrix} 140 & -50 & -30 \\ -50 & 100 & -40 \\ -30 & -40 & 90 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 140 & -50 & -30 \\ -50 & 100 & -40 \\ -30 & -40 & 90 \end{bmatrix}$$

$$= 140(9000 - 1600) + 50(-4500 - 1200) - 30(2000 - (-3000))$$

$$= 1036000 - 285000 - 150000$$

$$\Delta = 601000$$

$$\Delta_1 = \begin{vmatrix} 80 & -50 & -30 \\ -30 & 100 & -40 \\ 0 & -40 & 90 \end{vmatrix}$$

$$= 80(9000 - 1600) + 50(-2700 - 0) - 30(1200 - 0)$$

$$= 592000 - 135000 - 36000$$

$$\Delta_1 = 421000$$

$$\Delta_2 = \begin{vmatrix} 140 & 80 & -30 \\ -50 & -30 & -40 \\ -30 & 0 & 90 \end{vmatrix}$$

$$= 140(-2700) - 80(-4500 - 1200) - 30(0 - 900)$$

$$= -378000 + 456000 + 27000$$

$$\Delta_2 = 105000$$

$$\Delta_3 = \begin{vmatrix} 140 & -50 & 80 \\ -50 & 100 & -30 \\ -30 & -40 & 0 \end{vmatrix}$$

$$= 140(0 - 1200) + 50(0 - 900) + 80(2000 + 3000)$$

$$= 140(-1200) + 50(-900) + 80(5000)$$

$$= -168000 - 45000 + 400000$$

$$\Delta_3 = 1,87000$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{421000}{601000} = 0.7 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{105000}{601000} = 0.174 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{187000}{601000} = 0.311 \text{ A}$$

The loop currents are

|                         |
|-------------------------|
| $I_1 = 0.7 \text{ A}$   |
| $I_2 = 0.174 \text{ A}$ |
| $I_3 = 0.311 \text{ A}$ |